


1 Create a relative timing test bench for the following circuit called Gate3.

```

`timescale 1ns / 1ps
//simulation time unit is 1ns and resolution is 1ps
//Author: Jianjian Song
//Date: August 16, 2020
//Purpose: ECE433 example circuit
module Gate3 (
input All, Blink,
output Right, Left);
wire w1;
    not U1 (w1, All);
    nand U2 (Right, w1, Blink);
    or U3 (Left, Left, Blink);
endmodule

```

| All | Blink | Right | Left |
|-----|-------|-------|------|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 |

 

| Time | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 12 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 |
|-------|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| All | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Blink | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Right | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Left | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |


2 Create an absolute timing test bench for the following circuit called Gate3.

```

`timescale 1ns / 1ps
//simulation time unit is 1ns and resolution is 1ps
//Author: Jianjian Song
//Date: August 16, 2020
//Purpose: ECE433 example circuit
module Gate3 (
input All, Blink,
output Right, Left);
wire w1;
    not U1 (w1, All);
    nand U2 (Right, w1, Blink);
    or U3 (Left, All, Blink);
endmodule

```

| All | Blink | Right | Left |
|-----|-------|-------|------|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 |

 

| Time | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 12 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 | 31 | 32 | 33 | 34 |
|-------|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| All | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Blink | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Right | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Left | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |

3 Gate3 Circuits

3.1 Gate Level

```
module Gate3Gates (  
  input All, Blink,  
  output Right, Left);  
  wire w1;  
      not U1 (w1, All);  
      nand U2(Right, w1, Blink);  
      or U3 (Left, All, Blink);  
endmodule
```

3.2 Logic Expressions

```
module Gate3Expression (  
  input All, Blink,  
  output reg Right, Left);  
  
  always @(All, Blink) begin  
      Right <= ~(All&Blink);  
      Left <= All | Blink;  
  end  
endmodule
```

3.3 Truth Table

```
module Gate3Table (  
  input All, Blink,  
  output reg Right, Left);  
  
  always @(All, Blink)  
      case({All,Blink})  
        0: {Right,Left}=2'b10;  
        1: {Right,Left}=2'b01;  
        2: {Right,Left}=2'b11;  
        3: {Right,Left}=2'b11;  
      endcase  
endmodule
```

3.4 Assign statement

```
module Gate3Assign (  
  input All, Blink,  
  output Right, Left);  
  
  assign Right = ~(All&Blink);  
  assign Left = All | Blink;  
endmodule
```

4 Gate3 Test Benches

4.1 Relative Time Instants

```
module Gate3TestRelative;
reg all1, blink1; // Inputs
wire RightGates, LeftGates; // Outputs
wire RightBehavior, LeftBehavior;
wire RightTable, LeftTable;
wire RightAssign, LeftAssign;
wire NOT_output = Gate3GateChip.w1; //internal wire of a device under test (DUT)

    initial begin
// Initialize Inputs
    all1 = 0; blink1 = 0; #3;
    all1 = 1; blink1 = 0; #4;
    all1 = 0; blink1 = 0; #5;
    all1 = 0; blink1 = 1; #5;
    all1 = 0; blink1 = 0; #3;
    all1 = 1; blink1 = 1; #4;
    all1 = 0; blink1 = 0; #3;
    $stop;
    end

// Associate the test bench with a device under test (DUT)
Gate3Gates Gate3GateChip ( .Blink(blink1), .Left(LeftGates), .Right(RightGates), .All(all1));
    Gate3Expression Gate3ExpressionChip (all1, blink1, RightBehavior, LeftBehavior);
Gate3Table Gate3TableChip (all1, blink1, RightTable, LeftTable);
Gate3Assign Gate3AssignChip (all1, blink1, RightAssign, LeftAssign);


endmodule
```

4.2 Absolute Time Instants

```
module Gate3TestAbsolute;
reg all1, blink1; // Inputs
wire RightGates, LeftGates; // Outputs
wire RightBehavior, LeftBehavior;
wire RightTable, LeftTable;
wire RightAssign, LeftAssign;
wire NOT_output = Gate3GateChip.w1; //internal wire of a device under test (DUT)
initial fork
    #0 all1 = 0; #3 all1 = 1; #7 all1 = 0;
    #20 all1=1; #25 all1=0;
    #0 blink1 = 0; #12 blink1 = 1; #17 blink1 = 0;
    #20 blink1 = 1; #25 blink1 = 0;
    #28 $stop; join
// Associate the test bench with a device under test (DUT)
Gate3Gates Gate3GateChip ( .Blink(blink1), .Left(LeftGates), .Right(RightGates), .All(all1));
    Gate3Expression Gate3ExpressionChip (all1, blink1, RightBehavior, LeftBehavior);
Gate3Table Gate3TableChip (all1, blink1, RightTable, LeftTable);
Gate3Assign Gate3AssignChip (all1, blink1, RightAssign, LeftAssign);



endmodule
```

5 Gate3 Simulation Waveforms

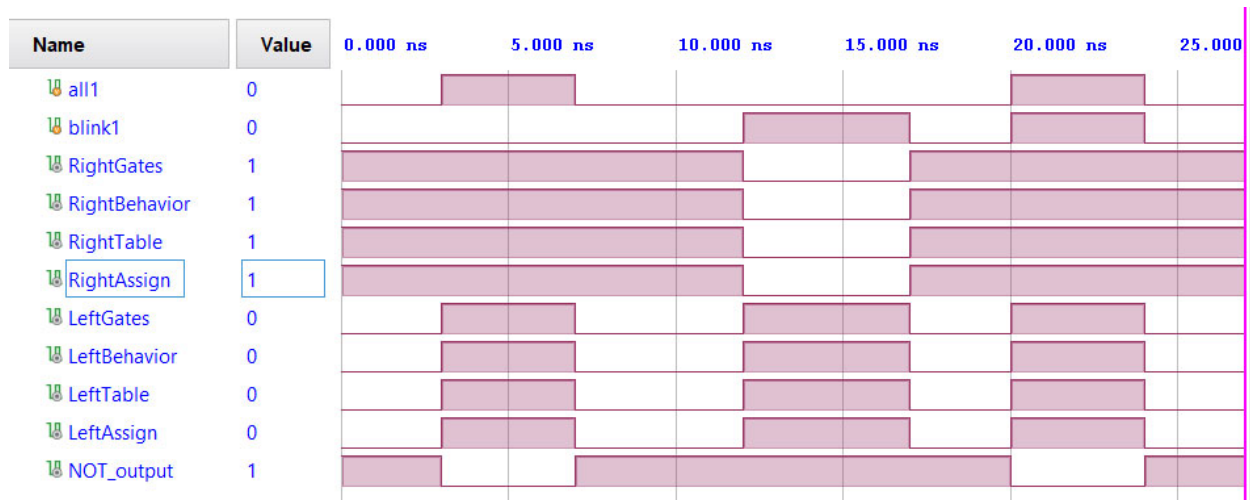

6 Gate3 Circuit with Zybo Board: gate3vivado

6.1 Zybo peripheral devices

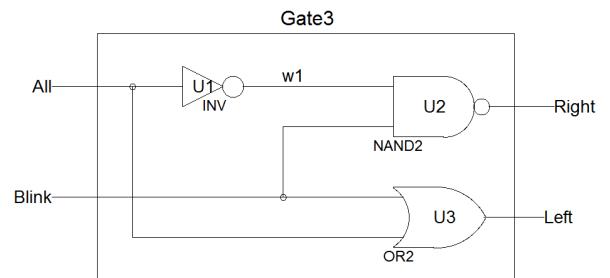 

6.2 Pin assignment in Xilinx device constraint file gate3vivado.xdc

```

##/File name: gate3vivado.xdc
set_property PACKAGE_PIN Y16 [get_ports All]
set_property PACKAGE_PIN R18 [get_ports Blink]
set_property PACKAGE_PIN G14 [get_ports Left]
set_property PACKAGE_PIN M15 [get_ports Right]
set_property IOSTANDARD LVCMOS33 [get_ports All]
set_property IOSTANDARD LVCMOS33 [get_ports Blink]
set_property IOSTANDARD LVCMOS33 [get_ports Left]
set_property IOSTANDARD LVCMOS33 [get_ports Right]

```

| I/O Ports | | | | |
|------------------|-----------|------|-----------|--|
| Name | Direction | Site | I/O Std | |
| All ports (4) | | | | |
| Scalar ports (4) | | | | |
| All | IN | Y16 | LVCMOS33* | |
| Blink | IN | R18 | LVCMOS33* | |
| Left | OUT | G14 | LVCMOS33* | |
| Right | OUT | M15 | LVCMOS33* | |


7 Verilog behavior implementation with a state machine.

7.1 Draw a state diagram and check it against the above test sequence

7.2 Create a Verilog Moore state machine for your state diagram

7.3 Create a test bench to test your state machine exhaustively

 7.4 Simulate your Verilog circuit to verify its correctness



```
module detect011StateMachineV1(X, Z, reset, CLOCK);
```

```
Endmodule
```

```

`timescale 1ns / 100ps

// File name      : detect011StateMachineV1.v
// Jianjian Song
// Fall 2020 HUST
// If the input X is 011 with 0 being the first bit, the output Z will produce a "1"
//the detection is recursive.

module detect011StateMachineV1(
input  X, RESET, CLOCK,
output reg Z,
// State variables
output reg [1:0] CurrentState);
reg [1:0] NextState;

// State codes
parameter      State1 = 2'b00, State0 = 2'b01, State011 = 2'b10, State01 = 2'b11;

// Output logic
always @ (CurrentState)
    if (CurrentState == State011) Z <= 1;
    else Z <= 0;

// State registers
always @ (posedge CLOCK)
begin
    if (RESET==1)
        CurrentState <= State1;
    else
        CurrentState <= NextState;
end

//next state logic
always@(CurrentState or X)
    case (CurrentState)
        State1: begin
            if (X==0) NextState <= State0;
            else NextState <= State1;
        end
        State0: begin
            if (X==0) NextState <= State0;
            else NextState <= State01;
        end
        State011: begin
            if (X==0) NextState <= State0;
            else NextState <= State1;
        end
        State01: begin
            if (X==0) NextState <= State0;
            else NextState <= State011;
        end
        default: NextState<=State1;
    endcase
endmodule

```

```

`timescale 1ns / 100ps

// File name      : detect011StateMachineV2.v
// Jianjian Song
// Fall 2020 HUST
// If the input X is 011 with 0 being the first bit, the output Z will produce a "1"
// The detection is recursive.

module detect011StateMachineV2(input X, RESET, CLOCK, output reg Z,
// State variables
output reg [1:0] CurrentState);



// State codes
parameter      State1 = 2'b00, State0 = 2'b01, State011 = 2'b10, State01 = 2'b11;

// Output logic
always @ (CurrentState)
    if (CurrentState == State011) Z <= 1;
    else Z <= 0;




// State registers
always @ (posedge CLOCK)
    if (RESET==1) CurrentState <= State1;
    else
        case (CurrentState)
            State1: if (X==0) CurrentState <= State0; else CurrentState <= State1;
            State0: if (X==0) CurrentState <= State0; else CurrentState <= State01;
            State011: if (X==0) CurrentState <= State0;          else CurrentState <= State1;
            State01: if (X==0) CurrentState <= State0; else CurrentState <= State011;
            default: CurrentState<=State0;
        endcase
endmodule

```

  
8 Draw a timing diagram in the grid paper to perform a manual timing simulation of the state diagram below.



9 Detect 011 Test Pattern Generation;

 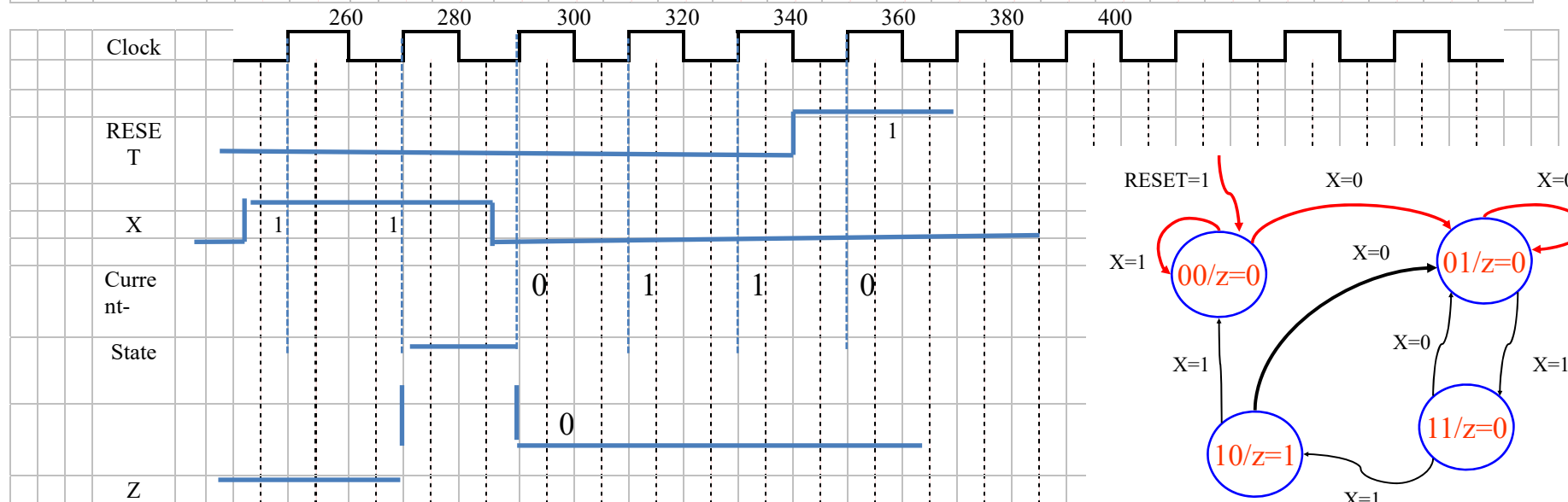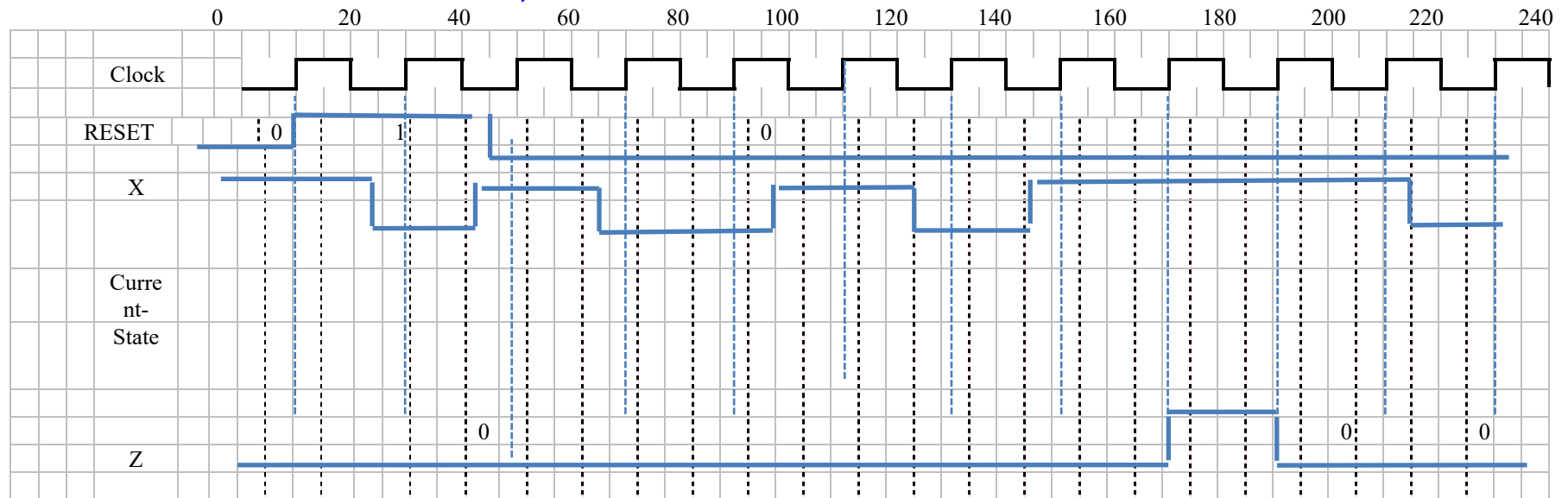

Notice how a periodic clock signal is generated.

```
`timescale 1ns / 100ps

// File name      : detect011TB.v
// Jianjian Song
//Fall 2020 HUST
// If the input X is 011 with 0 being the first bit,
//the output Z will produce a "1". The detection is recursive.

module detect011_test_circuit;
reg X, R, clk;
wire Zstate, Zexp, Zversion2;
wire [1:0] CurrentState,StateV2;
wire [1:0] Nextstate= UnitV1.NextState;
wire [1:0] StateExp= {UnitExpressions.QA,UnitExpressions.QB};

initial begin #0 clk=0; end          //initial value for input clock
always #10 clk=~clk;                //generate a periodic signal as clock


        initial fork                //absolute time instances
            #0 R=0; #15 R = 1; #43 R=0; #340 R=1;
            #0 X=1; #22 X=0; #42 X=1; #67 X=0;
            #103 X=1; #121 X=0; #143 X=1;
            #215 X=0; #242 X=1; #284 X=0;
            #380 $stop;

        join

detect011StateMachineV1 UnitV1(X, R, clk, Zstate, CurrentState);
detect011Expressions UnitExpressions(X, R, clk, Zexp);
detect011StateMachineV2 UnitV2(X, R, clk, Zversion2, StateV2);

endmodule
```

9.1 Vivado Simulation Results

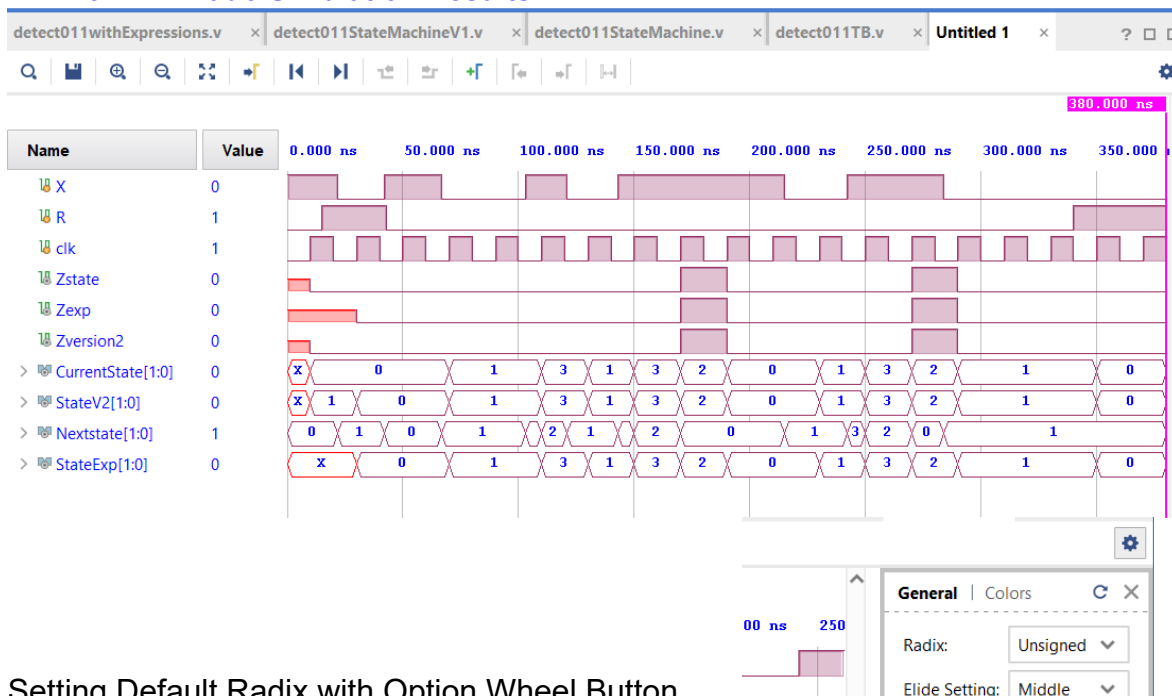

Setting Default Radix with Option Wheel Button.